



THE PAPUA NEW GUINEA UNIVERSITY OF TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND COMMUNICATIONS ENGINEERING

SECOND SEMESTER EXAMINATION – 2022

EE221: DIGITAL LOGIC SYSTEMS

BEEL2, BSAP2, BEBE2

TIME ALLOWED: 3 HOURS

INFORMATION FOR STUDENTS:

1. You have **TEN [10] MINUTES** to read through the paper. You must not begin writing during this time until you are told to.
2. Answer ALL **SIX QUESTIONS**. Attend to all the Examination Questions in any order.
3. All Answers must be written in the **ANSWER BOOK** supplied.
4. **COMPLETE THE DETAILS REQUIRED ON THE FRONT COVER OF YOUR ANSWER BOOKLET – DO THIS NOW!**
5. Only the drawing instruments and the calculators are permitted on your desk. Text books and notebooks and any electronic readers are **NOT** permitted.
6. If you are found cheating in the Examination, the penalties specified by the University shall apply.
7. **TURN OFF** all **Mobile Phones** and place them on the floor under your seat before the start of Examination.

“GOOD LUCK”

Question 1: [10 marks]

- A. Convert binary 1101.101 to its equivalent decimal number. [1 mark]
- B. Perform the following arithmetic operations;
- Add $4A_{16}$ with $3B_{16}$ [1 mark]
 - Subtract decimal 16 from 12 in binary. [1 mark]
- C. Name the two major types of logic circuits used in digital logic designs. [2 marks]
- D. The Exxon-Mobil PNG LNG in their chemical processing plant uses a microcomputer to monitor the temperature and pressure of four chemical tanks, as in Figure 1. Whenever a temperature or a pressure exceeds the danger limit, an internal tank sensor applies a 1 (High) to its corresponding output to the microcomputer. If all conditions are OK, then all outputs are 0 (Low).

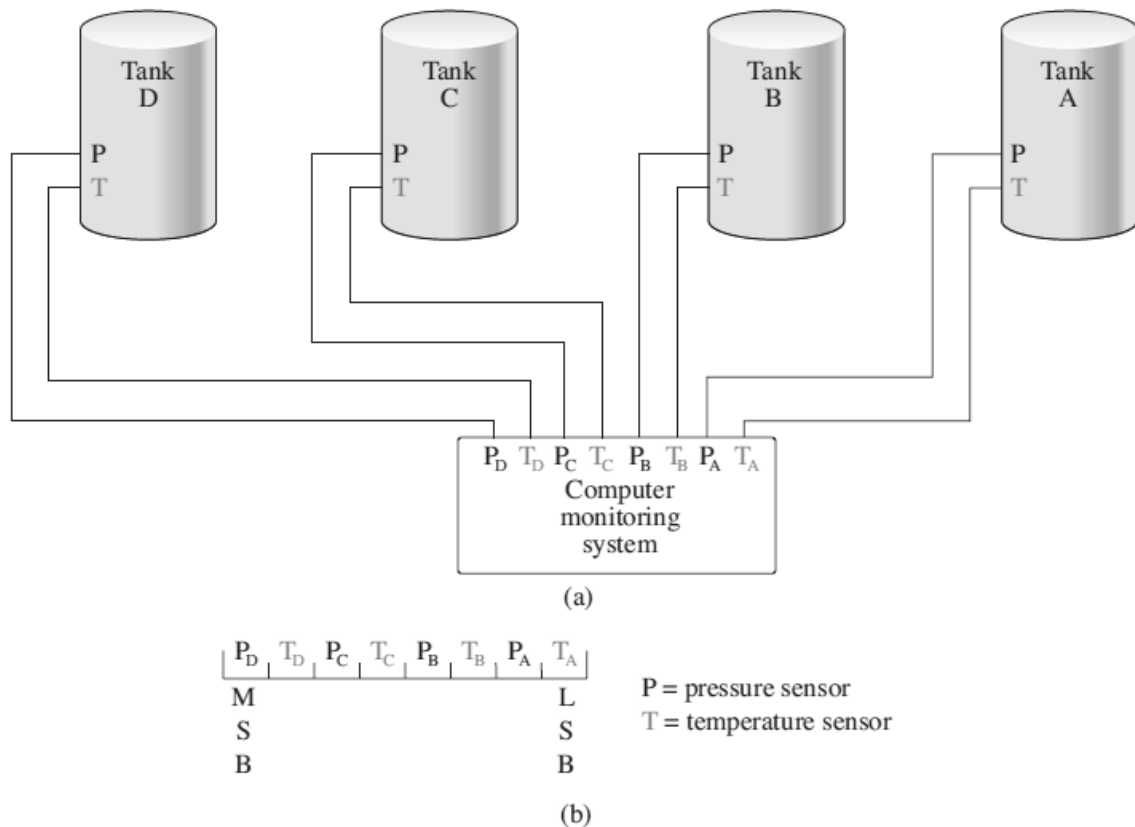


Figure 1. (a) Circuit connections for chemical temperature and pressure monitoring.
(b) Layout of binary data read by the computer monitoring system.

- If the microcomputer reads the binary string 0011 11102, what problem(s) exist? [1 mark]
- What problem(s) exist if the microcomputer is reading $A2_{16}$ ($A2_{Hex}$)? [1 mark]
- What hexadecimal number is read by the microcomputer if the temperature and pressure in tanks A and C are HIGH? [1 mark]
- What is the binary number read by the computer if temperature in tank B is HIGH and both temperature and pressure in tank D are HIGH? [1 mark]
- In another area of the plant, only three tanks (A, B, and C) have to be monitored. What hexadecimal number is read if tank A has a HIGH temperature and pressure? [1 mark]

Question 2: [10 marks]

A. Inside a certain Liquid Petroleum Gas (LPG) storage plant, each three tanks (A, B, C) are equipped with liquid level sensors. The level sensor in each tank produces a HIGH level only when the level of LPG in the tank drops below a specified point. Design a logical circuit that monitors the LPG level that activates an alarm (X) when the level in *any two or more* of the tank drops below the specified point.

i. Derive the Truth Table of the tank level monitoring. [2 marks]

A	B	C	X (Alarm)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

ii. From the Truth Table in *i*, derive the general Boolean expression for the activated alarm output. [1 mark]

iii. From the Truth Table in *i* and/or Boolean expression in *ii*, use K-map and/or algebraic reduction method(s) (*use only one method*) and simplify to its simplest equivalent expression. [2 marks]

iv. Draw the logic circuit diagram of the simplified expression in *iii*. [1 mark]

B. Consider the combinational logic circuit shown in Figure 1. [4 marks]

 


Figure 2: Combinational logic circuit.

Derive the Boolean expressions for the two outputs (F_1 and F_2).

- i. F_1
- ii. F_2

Question 3: [10 marks]

- A. Applying algebraic reasoning and De’Morgans theorems, for each circuit shown in Figure 3, prove mathematically if its output provides the **Ex-OR** function, the **Ex-NOR** function, or **neither**. [3 marks]

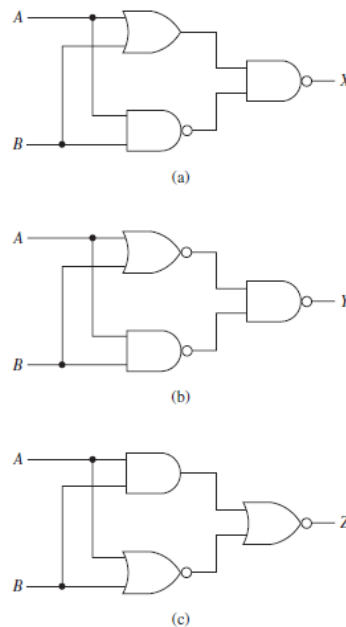


Figure 3: (a), (b) and (c).

- B. Figure 4 shows the summation operation and its characteristics truth table. It shows the full adder operation where A and B are the two inputs and additional C_{in} is the carry input from the previous addition of the least significant bit which was generated by the C_{out} (carry out). The Σ_1 is the sum output.

 


Figure 4: Addition in the more significant columns requires including C_{in} with $A_1 + B_1$.

- I. Completely fill in the Truth table. [1 mark]
- II. Determine the simplified algebraic expression of the sum (Σ_1) by;
 - i. From the Truth table in (I), derive the sum of product (SOP) terms of the Σ_1 . [1 mark]
 - ii. Use any or both of the logic circuit reduction techniques and simplify the SOP of the Σ_1 in (i)? [1 mark]

- III. Determine the simplified algebraic expression of the carry out (C_{out}) by;
- From the Truth table in (I), derive the sum of product (SOP) terms of the C_{out} . [1 mark]
 - Use any or both of the logic circuit reduction techniques and simplify the SOP of the C_{out} in (i)? [1 mark]
- IV. Finally, using the reduced logic expressions in (II) and (III) above, draw the combined and simplified logic circuit of the full adder. [1 mark]
- V. Name an advantage of reducing combinational circuits to its simplest. [1 mark]

Question 4: [10 marks]

- A. The internal circuitry of a positive-going-transition (PGT) edge triggered J-K flip-flop is show in Figure 5 below.

 


Figure 5. J-K Flip-flop internal circuitry.

- I. Determine the Q output function table of the clocked J-K flip-flop in Figure 5 above. [1 mark]

Table 1: J-K flip-flop function table

J	K	CLK	Q
0	0	↑	
1	0	↑	
0	1	↑	
1	1	↑	

- II. Complete the waveform of the Q output of the Figure 6 below based on the derived function table in Table 1 and Figure 5 above. [1 mark]

 


Figure 6. J-K Flip-flop internal circuitry.

B. Figure 7 (a), (b) and (c) shows the internal structure, truth table and symbol respectively of a level-triggered transparent D latch. Draw the Q output waveform of Figure 3 (d). [2 marks]

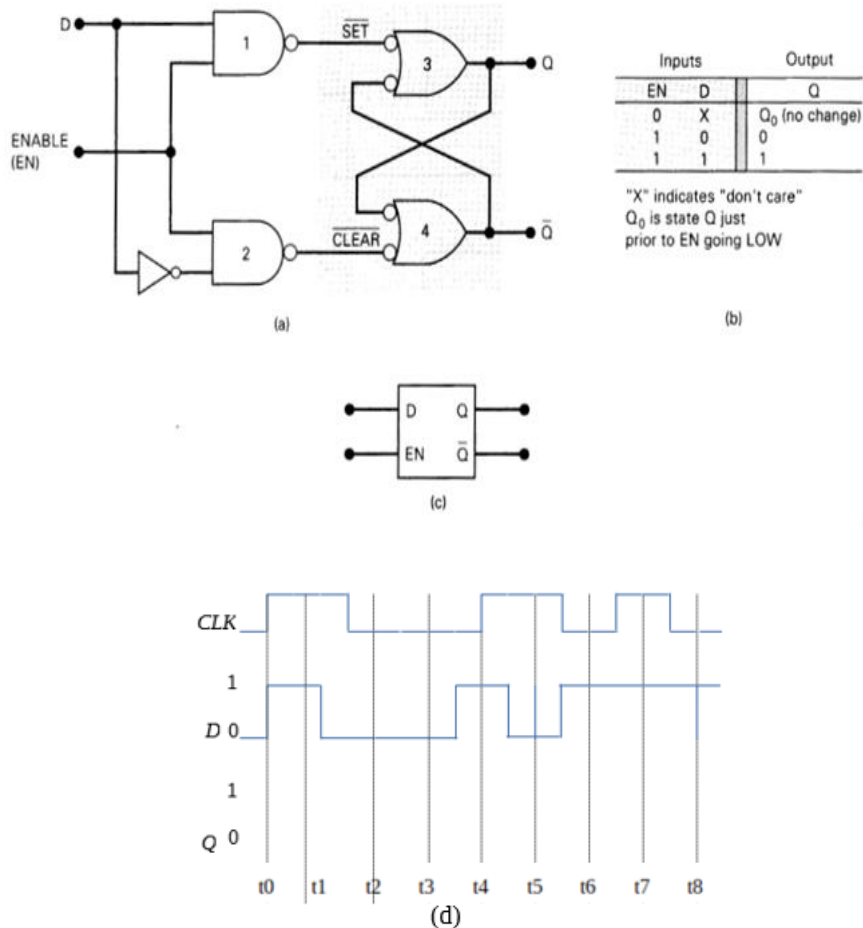


Figure 7. Transparent D latch: (a) structure, (b) truth table, (c) symbol, (d) waveform.

B. Figure 8 (a), (b) and (c) shows the symbol, function table and the internal structure of a gated S-R flip flop. Note that the S and R lines are the original Set and Reset inputs, however, with the addition of the AND gates, these S and R lines will be kept LOW-LOW (Hold condition) as

long as the Gate Enable is LOW. The flip-flop will operate normally while the Gate Enable is HIGH as can be seen in the function table and also indicated in the internal structure diagram.

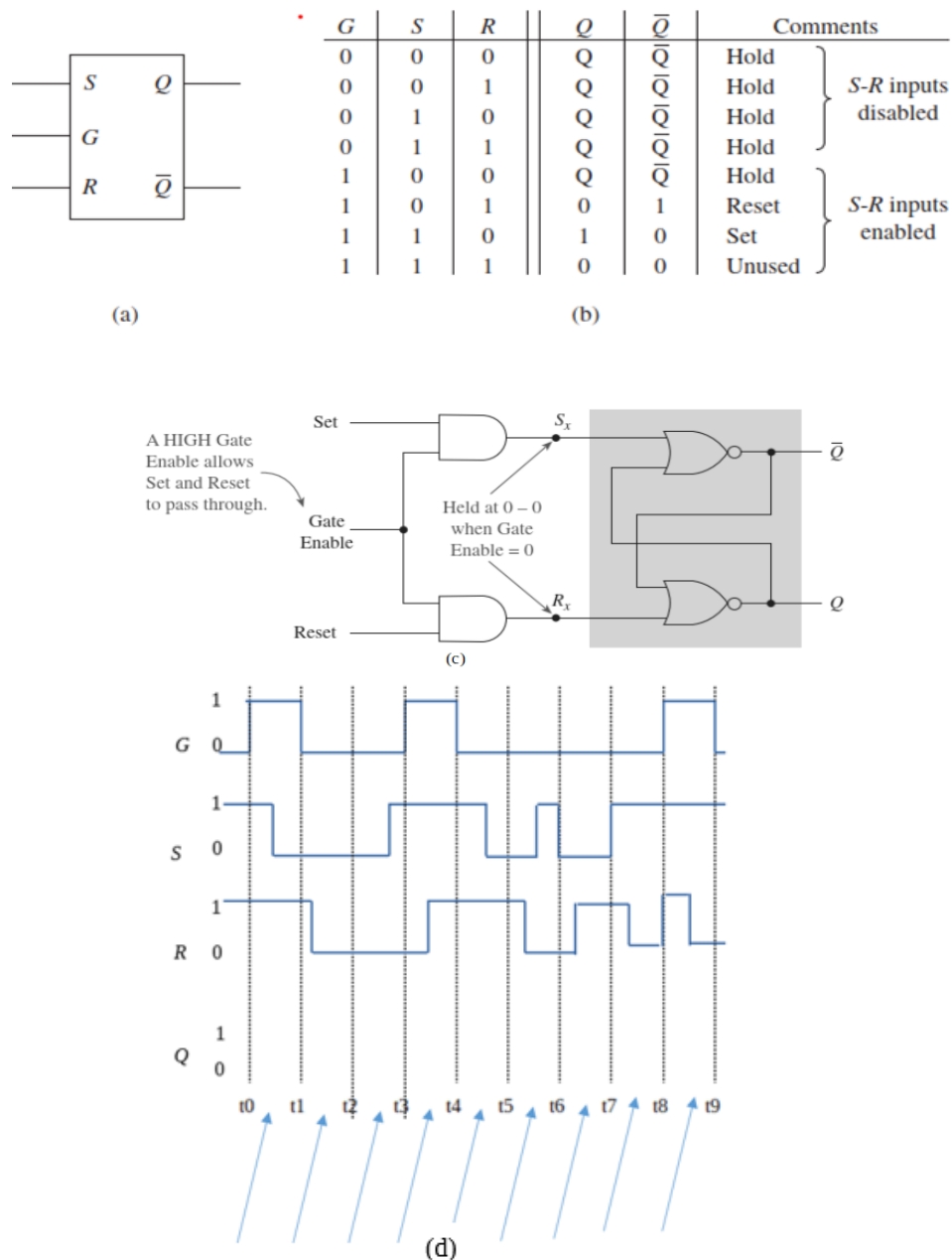


Figure 8. Gated S-R flip-flop: (a) symbol, (b) function table, (c) internal structure, (d) waveform

Feed the G , S , and R inputs into Figure 8 (d) of the waveform diagram into the gated S-R flip-flop in Figure 8 (c) by utilizing the input conditions of the function table in Figure 8 (b).

Question 5: [10 marks]

Block diagram of Figure 9 shows a Ripple MOD-32 up counter. The counter is implemented using five clocked J-K Flip-Flops; [Note: $J = K = 1$].

 


Figure 9: MOD-32 ripple up counter.

- Why is Clocked JK Flip-Flop used to implement counters and not D or S-R flip-flops? [1 mark]
- If Clocked J-K Flip – Flop with Asynchronous inputs are used to implement the MOD-32 up counter circuit as shown above, what must be done to the asynchronous inputs. [2 marks]
- Sketch a MOD 32 down counter circuit based on arrangement given in Figure 9 by using Clocked J-K Flip – Flop with Asynchronous inputs. [3 marks]
- Ripple Counters with MOD Number $<2^N$, where N is the number of Flip Flops. Sketch the circuit diagram of a Ripple MOD-27 UP COUNTER using five Clocked J-K F-F with Asynchronous inputs and NAND gates. [4 marks]

Question 6: [10 marks]

- The serial in serial out (SISO) **synchronous shift register** of a 3-bit data transfer circuit can be built using any flip-flop. Assuming a PGT shift pulse, D_2 , D_1 and D_0 as the data input and Q_2 , Q_1 and Q_0 as the data outputs:
 - Draw the block diagram with the correct number of flip-flops with input/output labeling. [2 marks]
 - Assuming the **synchronous shift register** you drawn in (i) has the binary number 101 to be transferred when shift pulse is applied. Complete the shifting of the 3-bits in Truth table below. The initial state is done for you assuming 000. [2 marks]

Clk	D	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0	0
1	$D_0 \rightarrow 1$				
2	$D_1 \rightarrow 0$				
3	$D_2 \rightarrow 1$				
4					
5					

- The block diagram of the serial in parallel out (SIPO) **synchronous shift register** of a 4-bit data transfer circuit can be developed using any of the flip-flop. Assuming a NGT shift pulse, D_3 , D_2 , D_1 and D_0 as the data inputs and Q_3 , Q_2 , Q_1 and Q_0 as the data output:
 - Draw the block diagram with the correct number of flip-flops with input/output labeling. [2 marks]
 - Assuming the **synchronous shift register** you drawn in (i) has the binary number 1110 to be transferred when shift pulse is applied. Complete the shifting of the 4-bits in Truth table below. The initial state is done for you assuming 0000. [2 marks]

Clk	D	Q ₀	Q ₁	Q ₂	Q ₃
0	0	0	0	0	0
1	D ₀ -> 0				
2	D ₁ -> 1				
3	D ₂ -> 1				
4	D ₃ -> 1				
5					

- iii. Represent the 4-bit SIPO synchronous shift register in a timing waveform. Correctly indicate the clock, input and output sequences when the shift pulse is applied. [2 marks]