



THE PAPUA NEW GUINEA UNIVERSITY OF TECHNOLOGY  
DEPARTMENT OF ELECTRICAL AND COMMUNICATIONS  
ENGINEERING

SECOND SEMESTER EXAMINATION 2021

EE222 ANALOG ELECTRONICS AND CIRCUITS

ELECTRICAL & COMMUNICATIONS ENGINEERING –  
YEAR 2 (BEEL)

TIME ALLOWED: THREE (3) HOURS

**INFORMATION FOR STUDENTS:**

1. You have **TEN (10)** minutes to read the paper.  
You must **NOT** begin answering during this time.
2. This is a closed book exam, only drawing instruments and calculators are allowed. No **ELECTRONIC DEVICES PERMITTED.**
3. There are 5 questions in this paper. Answer **ALL** questions.
4. All questions carry equal marks as shown. The paper is worth 50 marks.
5. If you are found cheating in the examination, the penalties specified by the University shall apply.
6. All **MOBILE** phones must be turned off before the start of the examination and remain **OFF** during examination period.

**QUESTION ONE: [3+5+2=10]**

- a) Calculate the intrinsic carrier concentration in germanium at  $T = 300$  K. Some parameters you may need for your calculation are provided below.

Semiconductor constants		
Material	$E_g$ (eV)	$B$ ( $\text{cm}^{-3} \text{K}^{-3/2}$ )
Silicon (Si)	1.1	$5.23 \times 10^{15}$
Gallium arsenide (GaAs)	1.4	$2.10 \times 10^{14}$
Germanium (Ge)	0.66	$1.66 \times 10^{15}$

Boltzmann's constant ( $k$ ) =  $(86 \times 10^{-6} \text{ eV/K})$   
 Electron charge,  $e = 1 \text{ eV} = 1.6 \times 10^{-19} \text{ joules}$

- b) Calculate the majority and minority carrier concentrations in germanium at  $T = 300$  K for:
- $N_d = 2 \times 10^{16} \text{ cm}^{-3}$  and
  - $N_a = 10^{15} \text{ cm}^{-3}$
- c) Current flow in a semiconductor are caused by two basic processes. What are the two processes and what causes the current flow in each case?

**QUESTION TWO: [5+5=10]**


- a) Calculate the built-in potential barrier,  $V_{bi}$ , for a Germanium pn junction at  $T = 300$  K for  $N_a = 10^{16} \text{ cm}^{-3}$  and  $N_d = 10^{17} \text{ cm}^{-3}$ .
- b) A silicon pn junction at  $T = 300$  K is doped at  $N_d = 10^{16} \text{ cm}^{-3}$  and  $N_a = 10^{17} \text{ cm}^{-3}$ . The junction capacitance is to be  $C_j = 0.8 \text{ pF}$  when a reverse-bias voltage of  $V_R = 5 \text{ V}$  is applied. Find the zero-biased junction capacitance,  $C_{j0}$ .

**QUESTION THREE: [4+6=10]**

- a) A silicon pn junction diode at  $T = 300$  K has a reverse-saturation current of  $I_s = 2 \times 10^{-12} \text{ A}$ . Determine the required forward-bias voltage to produce a current of
- $I_D = 50 \mu\text{A}$
  - $I_D = 1 \text{ mA}$ .

Assume  $n = 1$ .

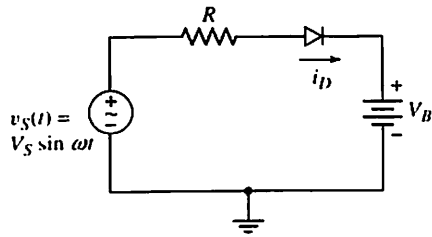- b) For the circuit given below, assume  $V_B = 4.5 \text{ V}$ ,  $R = 250 \Omega$ ,  $V_Y = 0.6 \text{ V}$ , and  $v_s(t) = 12 \sin \omega t$  (V).




Determine:

- (i) the peak diode current
- (ii) the maximum reverse-bias diode voltage
- (iii) the fraction of the cycle over which the diode is conducting.

**QUESTION FOUR: [5+5=10]**

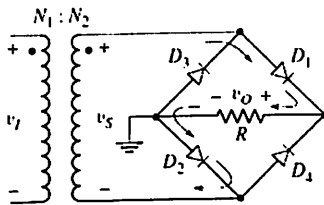- a) The bridge circuit shown below has an input voltage of  $v_s = V_M \sin \omega t$ . Assuming a diode cut-in voltage of  $V_Y = 0.7V$ , determine the fraction (percent) of time diode  $D_1$  is conducting for a peak sinusoidal voltage of  $V_M = 4 V$ .



- b) Assume the input signal to a rectifier circuit has a peak value of  $V_M = 12 V$  and is at a frequency of 60 Hz. Assume the output load resistance is  $R = 2 k\Omega$  and the ripple voltage is to be limited to  $V_r = 0.4 V$ . Determine the capacitance required to yield this specification for a (i) full-wave rectifier and (ii) half-wave rectifier.

**QUESTION FIVE: [10]**

Design a full-wave rectifier which will supply a peak output voltage of 12 V, deliver 120 mA to the load, and produce a ripple output of not more than 5 percent. The input line voltage for the rectifier will be 120 V (rms) at 60 Hz.

**EE222 ANALOG ELECTRONICS AND CIRCUITS  
EXAM AIDS – SEMESTER 2 FINAL EXAM 2021**

$$n_i = \sqrt[3]{2} e^{( )} \quad (1.1)$$

$$n_o p_o = n_i^2 \quad (1.2)$$

$$V_{bi} = \frac{kT}{e} \ln\left(\frac{N_a N_d}{n_i^2}\right) = V_T \ln\left(\frac{N_a N_d}{n_i^2}\right) \quad (1.16)$$

$$C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}}\right)^{-1/2} \quad (1.17)$$

$$i_D = I_S \left[ e^{\left(\frac{v_D}{nV_T}\right)} - 1 \right] \quad (1.18)$$

**Hints for Question 3 (b) and Question 4 (a):**

Solve using Kirchhoff's Voltage Law

$$i_D(\text{peak}) =$$

$$v_R(\text{max}) =$$

$$wt_1 =$$

$$\text{By symmetry, } wt_2 =$$

$$\text{Percentage time} =$$

$$V_r = \frac{V_M}{2fRC} \quad (2.9)$$

**Hints for Question 5:**

$$RL =$$

$$v_s(\text{max}) =$$

$$v_s(\text{rms}) =$$

$$N1/N2 =$$

$$V_r =$$

$$C =$$

$$i_{D,\text{peak}} \cong \frac{V_M}{R} \left( 1 + \pi \sqrt{\frac{2V_M}{V_r}} \right) \quad (2.21)$$

$$i_{D(\text{avg})} = \frac{1}{\pi} \sqrt{\frac{2V_r}{V_M}} \frac{V_M}{R} \left( 1 + \frac{\pi}{2} \sqrt{\frac{2V_M}{V_r}} \right) \quad (2.25)$$

PIV =