



THE PAPUA NEW GUINEA UNIVERSITY OF TECHNOLOGY  
DEPARTMENT OF ELECTRICAL AND COMMUNICATIONS ENGINEERING

FIRST SEMESTER EXAMINATION – 2022

EE312: ELECTRICAL MEASUREMENT & INSTRUMENTATION

BEEC3 and BEEP3

TIME ALLOWED: 3 HOURS,

INFORMATIONS FOR STUDENTS

1. You have **TEN [10] MINUTES** to read through the paper. You must not begin writing during this time.
2. Answer **FIVE QUESTIONS**. Attend to all the Examination Questions in any order.
3. All Answers must be written in the **ANSWER BOOK** supplied.
4. Make sure that you have a data sheet at the final page of the Exam Paper.
5. **COMPLETE THE DETAILS REQUIRED ON THE FRONT COVER OF YOUR ANSWERBOOK – DO THIS NOW.**
6. Only the drawing instruments and the calculators are permitted on your desk. Text books and notebooks are **NOT** permitted.
7. If you are found cheating in the Examination, the penalties specified by the University shall apply.
8. **TURN OFF** all **Mobile Phones** and place them on the floor under your seat before the start of Examination.

### **QUESTION1 [20 Marks]**

Attend to the following **TRUE OR FALSE** statements and answer them. Write on your answer sheet **True** if the statement is true or **False** if you think otherwise.

- (a)** In moving coil and moving iron instruments damping torque is significant for suppressing pointer oscillations.
- (b)** Electrodynamometer instruments are calibrated using DC source and operated on AC supply and are called transfer type instruments.
- (c)** Primarily, three torques encountered in moving iron and moving coil instruments are damping torque, control torque and braking torque.
- (d)** Torque responsible for moving pointer over the scale of a moving coil instrument is called control Torque.
- (e)** Systematic error influences accuracy.
- (f)** Random error influences precision of the instrument.
- (g)** Zero error and calibration error can be classified as types of random errors.
- (h)** Springs used to control motion of coil resulting in deflection is called hair spring and they are spirally wound, phosphor-bronze springs.
- (i)** PMMC Instrument can have only dc supply to the stationary coil.
- (j)** Shifting the histogram away from the expected value is an indication of low precision.
- (k)** Instrument Amplifiers are not preferred over OP Amps in sensitive applications to stop resistance of bridge to interfere with amplifier gain.
  - (l)** If the independent errors propagate linearly and are added linearly.
- (m)** Passive transducers require external excitation supply.
- (n)** Resistance temperature detector used for temperature measurement is an example of active transducer.
- (o)** Strain gage can be arranged in Wheatstone bridge so that the effect of disturbance introduced by environment temperature fluctuations can be nullified.
- (p)** If output voltage of a Wheatstone bridge is non-zero under null condition it can be zeroed by implementing an offset adjust circuit.
- (q)** In AC Bridges Reactance are not used for calibration, but quality factors.
- (r)** Impedance of an AC Bridge Arm in series does not have an equivalent parallel arrangement.
- (s)** Eddy current circulating through coil former contributes to damping by Lenz's Law.
- (t)** Sensitivity of a bridge is formulated under balanced condition.

## QUESTION2 [20 Marks]

Perform the following analysis described in (a) and (b) respectively. Question2 (a) is based on figure 1 and question 2 (b) is based on figure 2.

(a) Two strain gages are used to measure mechanical stress in a physical system. The transducers (figure 1a) are connected to DC bridge by configuration presented in figure 1 (b). Perform the following analysis.


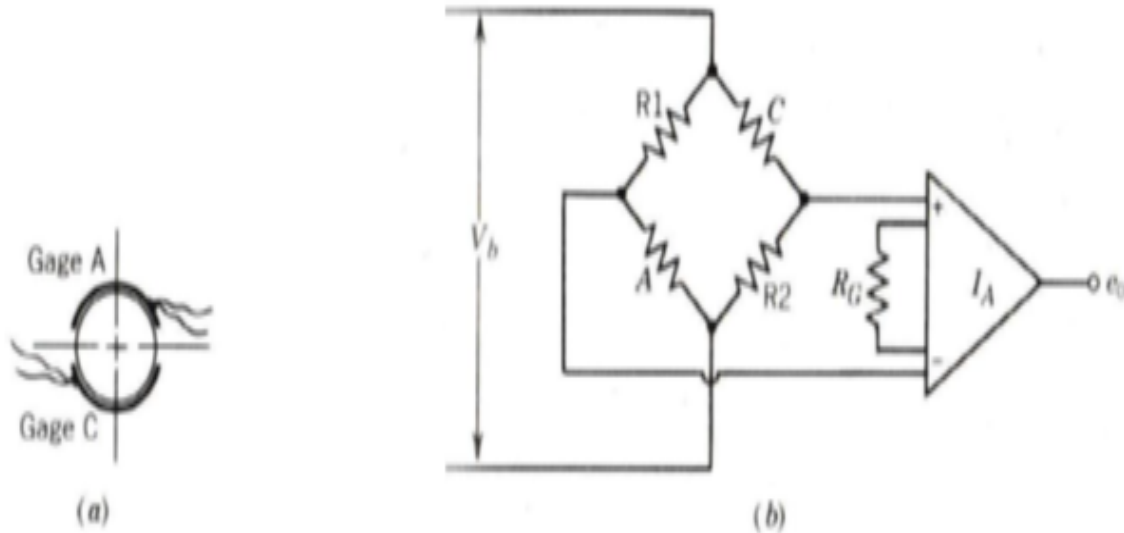


Figure1: For Question 2 (a)

- (i) State the mathematical relationship between stress, the change in length, length, the resistance and change in resistance of the elastic material.
- (ii) If  $V_B$  is supplied to the bridge, with bridge elements  $R_1$ ,  $R_2$ ,  $A$  and  $C$ ; derive the unbalanced voltage equation of the bridge.
- (iii) Express bridge arm resistance relationships from the null condition by making  $R_1$  the subject.
- (iv) From (ii), let  $A = C = R$ . If  $A$  undergoes a change of  $\Delta R$ , simplify the unbalanced voltage equation. What is the value of gauge factor ( $GF$ )?

(b) Derive necessary equations that summarize the conversion of measured differential pressure to differential voltage  $\Delta E$  as depicted in schematic diagram of **figure 2**. Express  $\Delta E = E_2 - E_1$  in terms of  $C_1$ ,  $C_2$ ,  $d$ , and  $x$  under unbalanced condition.

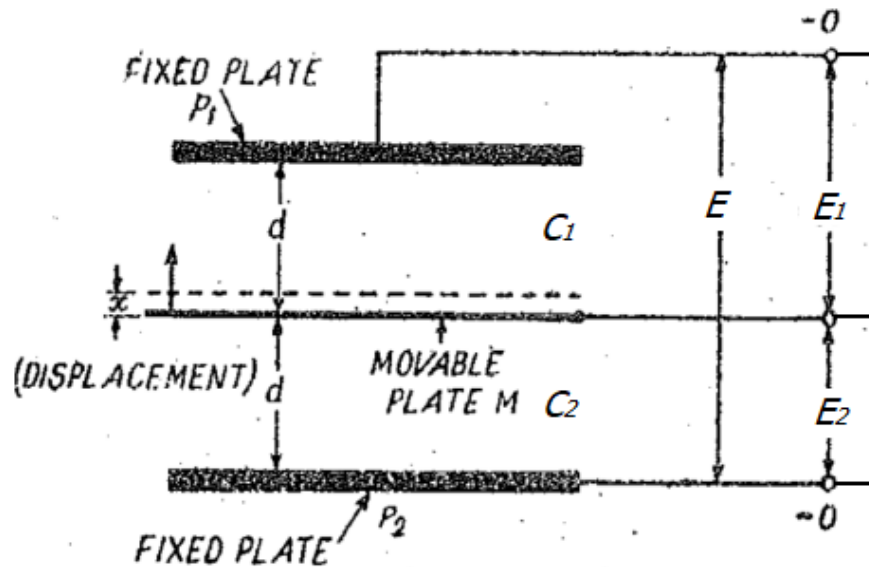

**Figure2:** For Question 2(b)


### QUESTION3 [20 Marks]

This question has parts (a), (b) and (c). All Parts are based on differential capacitive pressure transducers depicted in **figure 3**.

(a) A capacitive transducer uses two quartz diaphragms of area  $750 \text{ mm}^2$ . Upper and lower fixed plates are separated by a distance of  $3.5 \text{ mm}$  from the centre plate. A pressure of  $900 \text{ kN/m}^2$  when applied to the top diaphragm produces a deflection of  $0.6 \text{ mm}$  with respect to the centre diaphragm. The capacitance is  $370 \text{ pF}$  when no pressure is applied to the diaphragms.

Evaluate the following based on the differential capacitive transducer of **figure 3** after the application of a pressure of  $900 \text{ kN/m}^2$ .

- (i) Calculate the relative permittivity of dielectric material used in the capacitor transducer.
- (ii) Calculate effective value of capacitance  $C_{1x}$
- (iii) Calculate effective value of capacitance  $C_{2x}$

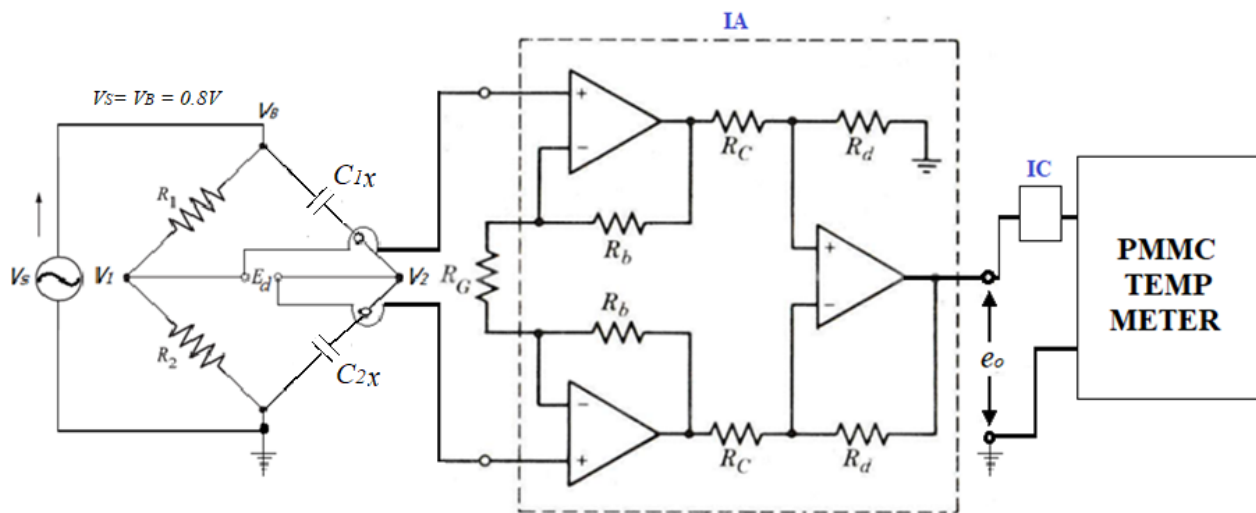

**Figure3:** For Question 3.


**(b)** The differential capacitor is connected to a Wheatstone bridge and difference amplifier as shown in **figure 3**. An AC supply of  $V_s = 0.8 \text{ V}$  is used to drive the bridge at a frequency of 50 kHz and the resistance of the bridge are  $R_1 = R_2 = 2500 \Omega$ . The precision Instrument Amplifier (IA) used in the **figure 3** has the following resistance rating. The resistances are  $R_G = 500 \Omega$ ,  $R_b = 1500 \Omega$ ,  $R_C = 100 \Omega$ , and  $R_d = 1000 \Omega$ .

- (i)** Write the expression for the unbalanced voltage equation of the Wheatstone bridge part of the circuit in **figure 3**.
- (ii)** Establish the relationship between the bridge arms elements at null (balanced) condition.
- (iii)** Calculate effective value of output voltage  $V_o$  when a pressure of  $900 \text{ KN/m}^2$  is imposed on the transducer.

**(c)** The voltage to current converter located between the IA and the meter has output current,  $I = e_o (10/R)$ , where  $R = 500 \Omega$ . The temperature meter provided is a PMMC instrument and has a coil of dimensions  $15 \text{ mm} \times 12 \text{ mm}$ . The flux density in the air gap is  $1.8 \times 10^{-3} \text{ wb/m}^2$  and the spring constant is  $0.14 \times 10^{-6} \text{ N-m/rad}$ . The scale for indication is to be calibrated at  $1.5^\circ\text{C}/1^\circ$ . Determine the number of turns required to produce an angular deflection for  $150^\circ\text{C}$  temperature reading.

#### QUESTION4 [20 Marks]

A four-arm ac “parallel inductance bridge” is shown in **figure 4**. The bridge operated at 1 kHz, is at null. The bridge impedance are;  $Z_{DA} = 1500 \Omega$ ,  $Z_{BC} = 1\ 000 \Omega$ ,  $Z_{CD} = 10 + 1 / j\omega 10^{-7} \Omega$  and  $Z_{AB} = 1/R_x + 1/jX_x$ . Resistance  $R_x$  is the equivalent parallel resistance and  $X_x$  is equivalent parallel Reactance.

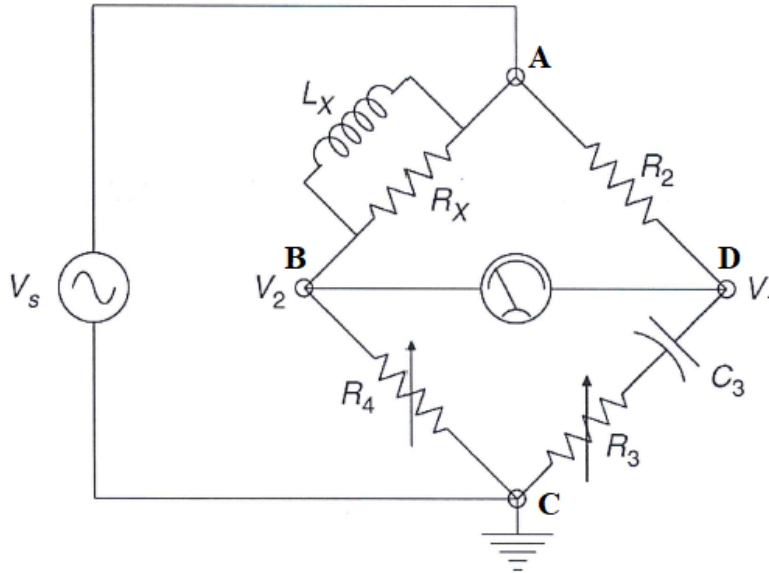


**Figure 4:** For Question 4

Perform the following analysis based on the above information.

- Without substituting the numerical values, establish the expression for resistance  $R_x$  and the expression for reactance  $X_x$  at null.
- Derive the expression for the effective Inductance  $L_x$ .
- Derive the expression for the Quality Factor ( $Q_p$ ) for the bridge of **figure4**.
- Calculate the value for Quality factor ( $Q_p$ ) at Null.
- Calculate the effective value of inductance  $L_x$  at null.
- Calculate the effective resistance value for resistor  $R_x$  at null.

### QUESTION5 [20 Marks]

An electro-dynamometer Wattmeter shown in **figure 5** is used to measure power in an AC electrical circuit. The load voltage is 200 V and the instrument has total resistance of the voltage coil circuit as  $9300 \Omega$ . The inductance of the voltage coil is 25mH. The mutual inductance changes uniformly from  $-250 \mu\text{H}$  at zero deflection to  $+250 \mu\text{H}$  at full scale. A current of 25 Amps with a lagging power factor of 0.75 flows through the load. When subject to maximum load current the angle of full scale deflection being  $120^\circ$ .

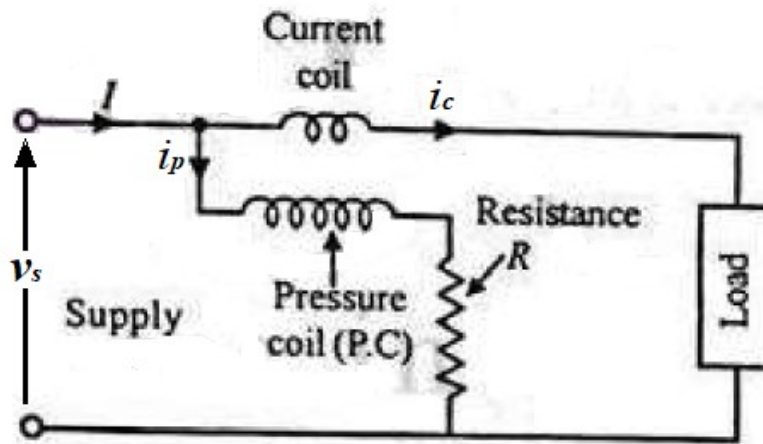

**Figure 5:** For Question 5.

The resistance of current coil is negligible in comparison to resistance  $R$ . A pair of hair spring with elastic constant of  $4.63 \times 10^{-6} \text{ N-m/rad}$  is used to control the instrument's deflection.

Perform the following calculations;

- Calculate the current flowing through voltage coil and express your answer as rms current.
- Calculate the deflection torque when 25 Amps of alternating current flows through the load.
- Determine the angle of deflection when 25 Amp of current is drawn by the load.
- What could the value for the maximum rating in Amps of the scale be?

**FINAL PAGE OF EXAMINATION QUESTION**