



THE PAPUA NEW GUINEA UNIVERSITY OF TECHNOLOGY

**DEPARTMENT OF ELECTRICAL AND COMMUNICATIONS
ENGINEERING**

SECOND SEMESTER EXAMINATION (2022)

EE324 – ELECTRICAL MACHINES AND DRIVES

BEEP3

TIME ALLOWED: 3 HOURS

INFORMATION FOR STUDENTS:

- You have TEN (10) minutes to read the paper. You must NOT begin writing during this time.
- All answers must be written in the ANSWER BOOK supplied. COMPLETE THE DETAILS REQUIRED ON THE FRONT COVER OF YOUR ANSWER BOOK. DO THIS NOW.
- Drawing instruments and calculators are permitted.
- Answer ALL FIVE (5) questions. Total of 100 marks.
- All questions carry equal marks.
- If you are found cheating in the examination, the penalties specified by the University shall apply.
- Switch OFF all mobile phones.

QUESTION ONE

[3+6+2+9 = 20 marks]

- A. State three (3) methods of braking and/or reversing DC motors
- B. Name and explain two (2) speed control methods in DC motors .
- C. State the two (2) torque measurement techniques in DC motors.
- D. DC generators are named after the type of excitation. Under self-excitation, there are three (3) main excitation methods used.
 - I. Define **series** and **shunt generators** in terms of how the windings are connected.
 - II. State a distinction between each in terms of their **terminal voltage** and **load current**.

QUESTION TWO


[8+12 = 20 marks]

- A. An ideal transformer has a 150-turn primary and 900-turn secondary. The primary is connected to a 240-V, 50-Hz source. The secondary winding supplies a load of 3 A at a lagging power factor (pf) of 0.8.
Determine;
 - a) the a-ratio
 - b) the current in the primary
 - c) the power supplied to the load
 - d) the flux in the core.
- B. A 100-kVA, 13.2/2.2-kV, 50-Hz, step-down transformer has a core-loss equivalent resistance of 8 k Ω and a magnetization reactance of 7 k Ω . The equivalent winding impedance as referred to the primary side is $3 + j12 \Omega$.
If the transformer delivers the rated load at a power factor of 0.707 lagging, determine its voltage regulation and efficiency.

QUESTION THREE



[3+17 = 20 marks]

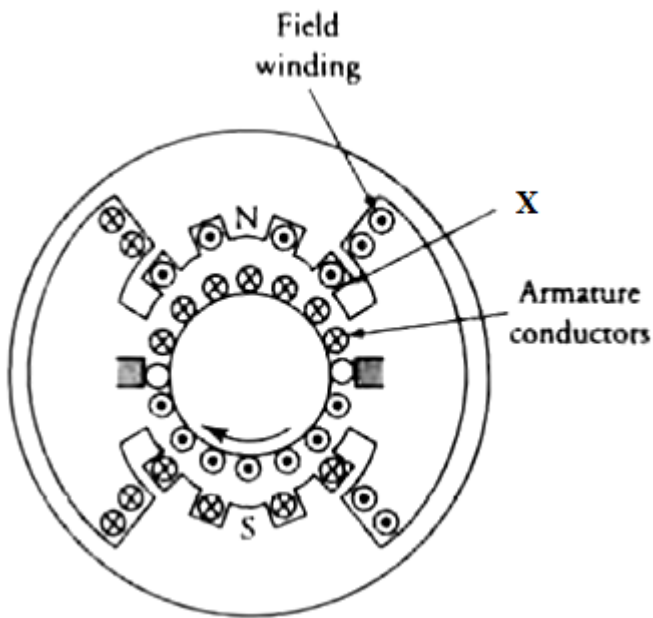A. The following is a diagram showing the cross-section of a DC generator.



- I. Name the component labelled X
- II. State the function of X

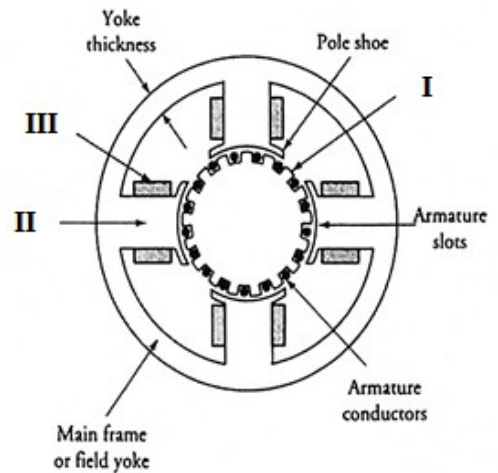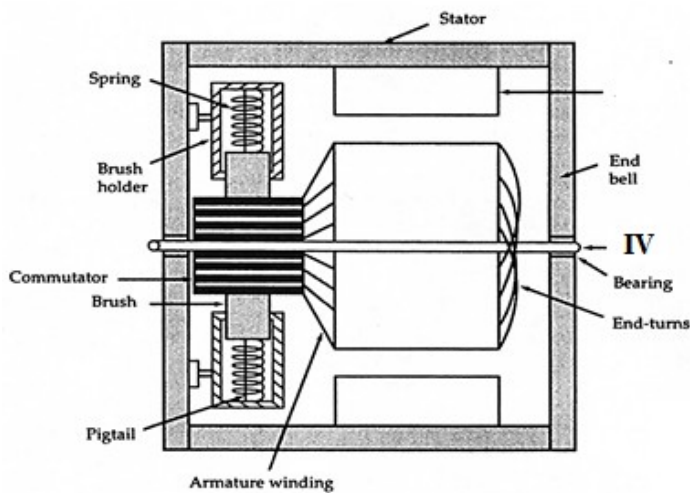B. The following figures are of a typical DC generator



- I. Name the parts labelled in roman numerals
- II. State the functions of the following
 - a) Commutator
 - b) Spring
- III. What material is the **brush** made of and why?

- IV. In an experimental setup, there appears to be a distortion in the main field windings, thereby reducing the emf induced in the armature coils.
- State one likely cause of the above
 - State two (2) ways in which the effect in (a)) can be reduced or minimized


QUESTION FOUR [12+8 = 20 marks]

A. The armature of a 6-pole, lap-wound dc generator has 28 slots with ten conductors in each slot. The flux per pole is 0.05 Wb and the armature speed is 1200 rpm.

Calculate;

- the frequency of the induced emf in each armature conductor,
- the induced emf in the armature,
- the induced emf per coil,
- the induced emf per turn, and
- the induced emf per conductor.

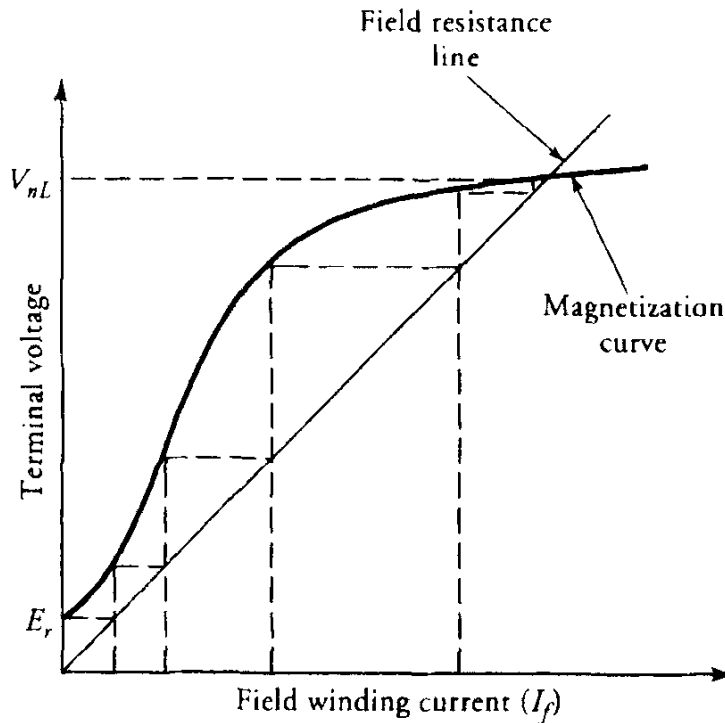B. The following diagram shows the voltage build-up phenomena.




- Explain the phenomenon with the aid of the graph
- State the factor that reduces or brings down voltage build-up

III. How does voltage build-up stop?

QUESTION FIVE

[14+6 = 20 marks]

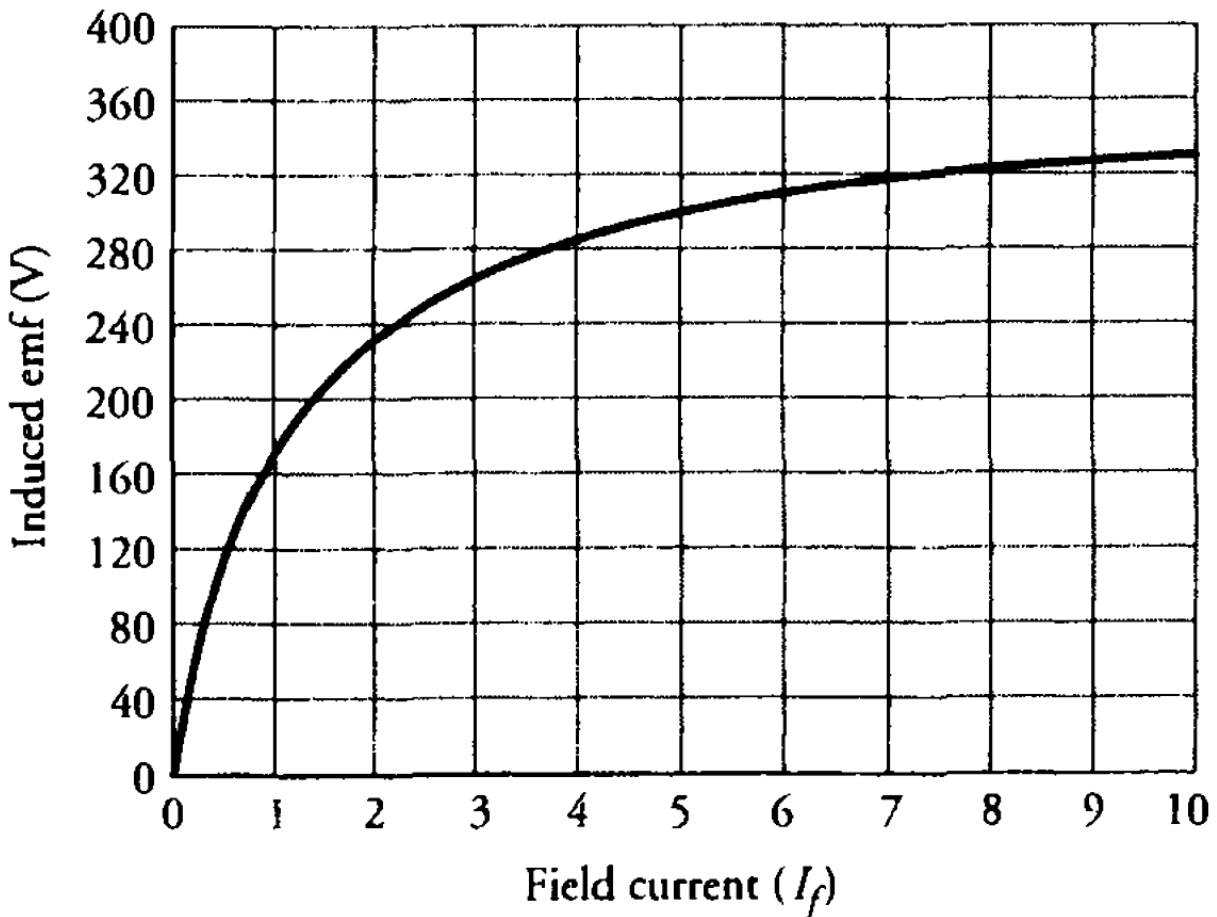A. A 240-kW, 240-V, 6-pole, 600-rpm, separately excited generator is delivering the rated load at the rated voltage. The generator has $R_a = 0.01 \Omega$, $R_{fw} = 30 \Omega$, $V_f = 120 \text{ V}$, $N_f = 500$ turns per pole, and $P_r = 10 \text{ kW}$. The demagnetizing mmf due to armature reaction is 25% of the armature current. Its magnetization curve is given in the figure below. [Only two (2) iterations required]




Determine;

- I. the induced emf at full load,
- II. the power developed,
- III. the torque developed,
- IV. the applied torque,
- V. the efficiency,

- VI. the external resistance in the field winding, and
- VII. the voltage regulation.

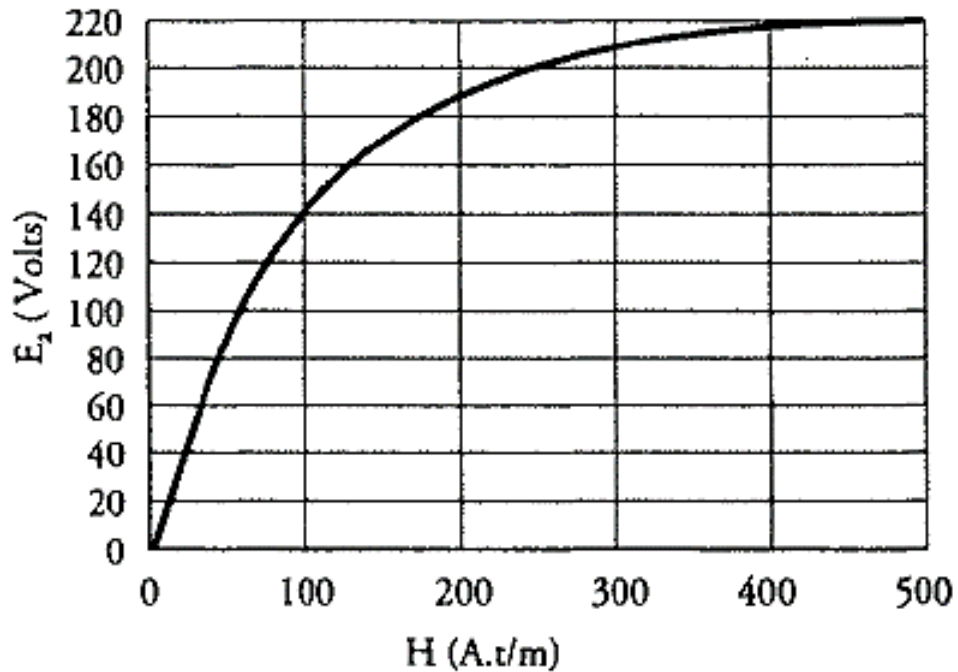B. The magnetization curve of a 10-hp, 220-V series motor is given in the figure below at 1200 rpm. The other parameters of the series motor are $R_a = 0.75 \Omega$, $R_s = 0.25 \Omega$ and $P_r = 1.04 \text{ kW}$.



- I. What is the armature current when the motor delivers its rated load at 1200 rpm?
- II. What is the efficiency of the motor at full load?
- III. What is the number of turns per pole?